1997
VOLUME 1

SELECTION GUIDES AND FUNCTION INDEX

IC MASTER

- Master Selection Guides
  Function Index

MASTER SELECTION GUIDES I

- Digital
- Digital Signal Processing
- Microprocessor
- Microprocessor Development Systems
- Interface
- Linear
- Memory

VOLUME 2
Selection Guides II
Military Parts
Application Notes
Alternate Source Directory

VOLUME 3
Manufacturers and Distributors Directory
Part Number Guide
Part Number Index
Advertisers Technical Data

Hearst Business Publishing/UTP Division

AC Controllers - Butterworth Filters

Function	Page-Line
A	
AC Controllers	1035-6
A/D Converters	
Binary	612-1
Decimal	664-1
DSP	282-96
A-Law	1015-138
Accelerometer	1011-1
Accumulators–See Digital Arithmetic	
ACE	478-39
Adder's–See Digital Arithmetic	
AF	
Pre-Amplifier	835-97
AGC	
Amplifiers	802-3
Television	856-6
ALU	282-13
AM	841-3
AM/FM	841-35
Amplifiers	
Antilog	804-54
Audio	802-55
Buffer	802-60
Current	803-11
Current Followers	863-1
Darlington	808-6
Differential	803-48
Headphone	833-7
Hearing Aid	833-14
Instrumentation	864-1
Intermediate Frequency	806-40
Isolation	804-25
Log	804-100
Loudspeaker	802-23
Operational–See Operational Amplifiers	
Power	833-97
Pre-Amplifier	835-97
Programmable Gain	805-52
Remote Control	845-62
Sense	752-1
Transimpedance	805-88
Variable Gain	806-7
Video	806-17
Analog Multipliers	802-44
Analog Shift Register	1035-41
Analog Switches	
Switches with Drivers	602-1
Switches without Drivers	606-45
Multiplexers	607-65
ARCNET	467-76
ARINC	735-3
ARINC 629	154-45
Arithmetic Functions–See Digital Arithmetic	
Arrays	
Darlington Transistor	808-6
Gate	2036-1
Linear/Digital	2068-1
Standard Cells	2071-1
Transistor	808-56
ASIC/Custom	2010-1
Asynchronous Transfer Mode (ATM)	1025-40
Attenuators	
Digital	830-60
Audio	830-89
Automotive	
Accelerometer	837-111
Alternator Voltage Regulator	837-116
Battery Charger	838-5
Electronic Ignition Circuit	838-48
Voltage Regulator	839-37
Wiper Control	839-42
B	
Ballast Controller	1035-79
Bar Code	1035-80
Battery Backup Circuit	478-45
Battery Charger	838-3
Battery Monitor	862-24
Baud Rate Generator	226-1
Bell 103/212/208A/B–See Telecommunications	
Bilateral Switch	154-48
Bilingual Processor	851-12
Bit Rate Generator	154-52
Boosters Current Followers	863-1
Buffers–See Digital Buffers	
Buffer Amplifiers	802-60
Bus–See Line Circuits	
Bus–Oriented Circuits–See Digital Bus-Oriented	
Butterworth Filters	1014-13

Function	Page-Line

C

Calculator Circuits.....839-54
Camera
Circuits..... 839-74
Traffic.....855-29
Cassette
Audio..... 848-15
VCR..... 849-24
CATV.....851-27
CCD
Camera.....839-75
Driver's..... 742-16
CCITT V.24.....717-5
CCITT V.28.....717-16
CD Player Circuits..... 831-38
CD ROM Circuits.....831-82
..... 862-27
Character Generator.....1102-1
Chip Sets..... 2202-1
Chroma Circuits–TV.....851-87
Clock
Automotive.....838-8
Generator..... 811-28
Microcomputer.....811-50
Microprocessor
Real Time..... 483-6
Oscillators/Dividers.....151-18
Code Identification System..... 154-57
Codecs
DSP..... 284-104
Telecom..... 1015-119
Color
Bar Generator.....851-122
Palette..... 479-54
.....857-23
Space Converter..... 154-58
TV Circuits.....850-103
Communications..... 2202-3
Comb Filter..... 851-137
Compandor
Telephone.....1017-34
Comparators
Address CMOS.....102-90
Linear
Dual..... 821-44
Quad.....825-52

Function	Page-Line

Single.....819-1
Phase..... 125-149
.....815-63
Consumer Circuits
Audio..... 830-1
Automotive.....837-111
Calculator..... 839-54
Camera.....839-74
Cellular 1031-92
Clock/Watch..... 839-104
Music..... 839-119
Radio
AM..... 841-3
AM/FM..... 841-35
FM..... 842-63
Remote Control..... 845-57
Speech 846-98
Tape Recorder
Audio..... 848-15
VCR.....849-24
Television..... 850-103
Controller
Ballast..... 1006-104
BUS, 1553/1750..... 481-79
Color Generator.....468-6
CRT..... 468-64
..... 857-74
Display.....469-25
Dynamic RAM.....469-43
Floppy Disk.....470-64
GPIB-Interrupt..... 470-114
Keyboard..... 471-77
LCD..... 472-5
..... 709-4
Motor..... 746-72
Mouse.....472-89
PCMCIA.....473-55
Power Factor..... 1007-87
Printer.....473-102
Programmable.....473-106
SCSI..... 474-83
.....483-26
Serial Communication..... 475-7
Stepper Motor.....475-77
Video..... 476-10
VMEBus.....476-34
Winchester.....476-51
Controls
Motor Speed
Recorders..... 848-57

Converters - Digital

Function	Page-Line
Remote	845-159
SCR	1038-17
Converters	
AC to DC	976-12
Analog to Digital	612-1
Digital to Analog	665-1
DC to DC	977-1
Flash	612-5
RMS to DC	976-20
Voltage to Current	1009-63
Voltage to Frequency	1009-72
Convolver	282-20
Cordless Telephone	1031-98
Correlator	282-31
Count Extenders for Prescalers	814-66
Counters	
Digital--Special	226-7
Frequency	841-63
CRC	715-4
Crosspoint Switches	1017-70
CRT Circuits	468-60
	857-74
Current	
Amplifiers	803-11
Boosters	863-1
Drivers	742-78
Source	1035-120
Custom Capabilities Charts	2010-1

D

D/A Converters	
DSP	283-3
General	665-1
Video	474-17
	482-115
D-Type Flip flops–See Digital Flip Flops	
Darlington Transistor Array	808-8
Data Acquisition	
Controller	706-8
Microprocessor	
General	479-88
Systems	706-9
Data Compression	479-126
Data Bus Circuits	735-1
Data Encryption	469-11
Data Selector–See Multiplexers	
Data Separator–Floppy Disk	470-102
Decoders–See Digital Decoders	
Display Drivers	708-1
FM	845-30
Keyboard	716-1
PLL Circuits-Tone	816-109
Delay	
Element	221-12
Delay Lines	
Digital	
CMOS	128-7
ECL	164-92
TTL	192-111
Delta Modulation	
Consumer	846-102
Telecom	1018-78
Demultiplexer	
Analog-CMOS	154-34
Digital-CMOS	149-120
Detector	
Fluid	1011-10
Level	1011-11
Phase-Frequency	222-16
Proximity	1037-102
Smoke	862-87
	1038-48
SSB	841-24
Dialers–See Telecommunications	
Digital	
BiCMOS	
Arithmetic	157-1
Buffers	157-5
Bus-Oriented Circuits	158-34
Decoders	160-100
Drivers	160-101
Flip-Flops,D	161-10
Gates	161-106
Inverters	158-33
Latches	162-1
Miscellaneous	162-111
Shift Registers	162-93
Transceivers, Bus	162-100
CMOS	
Arithmetic Functions	102-1
Buffers	105-6
Bus-Oriented Circuits	110-79
Counters, Binary	121-23
Counters, Binary Up/Down	123-168
Counters, Decade	124-12
Counters, Misc.	125-124

Function	Page-Line
Decoders	126-30
Delay Lines	128-107
Drivers	130-84
Flip-Flops, D	131-79
Flip-Flops, J-K	136-1
Gates, AND	136-172
Gates, AND-OR	139-162
Gates, Exclusive	141-145
Gates, Misc	142-81
Gates, NAND	137-178
Gates, NOR	140-132
Gates, OR	139-192
Inverters	109-26
Latches	142-92
Memories	146-54
Miscellaneous	154-33
Multiplexers	147-56
Multivibrators	150-106
Oscillators/Dividers	151-18
Shift Registers	151-59
Translators	154-7
ECL III/MISC.	
Counters	175-1
Flip-Flops, D	175-9
Flip-Flops, R-S	175-11
Gates	175-12
Latches	175-20
Miscellaneous	175-30
Multivibrators	175-21
ECL 10K	
Arithmetic Functions	164-1
Buffers	164-25
Bus-Oriented Circuits	164-39
Counters	164-60
Counters, Binary	164-64
Counters, Decade	164-74
Decoders	164-77
Delay Lines	164-92
Drivers	167-59
Flip-Flops, D	168-5
Flip-Flops, J-K	168-32
Gates	168-38
Inverters	164-34
Latches	168-131
Memories	169-19
Miscellaneous	170-38
Multiplexers	169-50
Multivibrators	169-99
Shift Registers	169-100
Translators	169-122
ECL 100K	
Arithmetic Functions	171-40
Buffers	171-52
Bus-Oriented Circuits	171-66
Counters	171-75
Decoders	171-82
Delay Lines	171-84
Drivers	172-66
Flip-Flops, D	173-7
Flip-Flops, J-K	173-30
Gates	173-32
Inverters	171-65
Latches	173-64
Memories	173-74
Miscellaneous	174-71
Multiplexers	173-76
Shift Registers	173-116
Translators	174-18
ECL 101K	
Arithmetic Functions	174-120
Miscellaneous	174-121
GaAs	
Buffers	176-1
Miscellaneous	176-15
HNIL/HTL	
Buffers/Inverters	177-1
Counters	177-4
Drivers	177-5
Flip-Flops, J-K	177-6
Flip-Flops, R-S	177-7
Gates	177-8
Miscellaneous	177-16
Multivibrators	177-15
SPECIAL	226-1
TTL	
Arithmetic Functions	178-1
Buffers	179-169
Bus-Oriented Circuits	182-114
Counters, Binary	187-105
Counters, Binary Up	187-118
Counters, Binary Up/Down	188-155
Counters, Decade	189-102
Counters, Decade Up	189-124
Counters, Decade Up/Down	190-88
Counters, Misc	190-174
Decoders	191-20
Delay Lines	192-111

DSP - Drivers

Function	Page-Line
Drivers	202-131
Flip-Flops, D	203-69
Flip-Flops, J-K	205-146
Gates, AND	207-15
Gates, AND/OR	210-207
Gates, AND/OR/Invert	211-11
Gates, Ex. NOR	213-83
Gates, Ex. OR	213-7
Gates, NAND	208-42
Gates, NOR	212-36
Gates, OR	211-170
Gates, OR/NOR	213-1
Inverters	181-113
Latches	213-103
Memories	215-44
Miscellaneous	221-6
Multiplexers	215-101
Multivibrators	218-78
Shift Registers	218-140
Transceivers, Bus	220-188
Translators	221-3
Digital Signal Processors	
Chip Sets	2204-14
Fixed Point	272-1
Floating Point	279-1
System Components	
Arithmetic Functions	282-1
Converters, A/D	282-96
Converters, D/A	283-4
Miscellaneous	284-73
Processors	283-45
	479-145
Registers	284-27
Digitally Controlled Potentiometers	227-6
Digital Telephone Circuits	1032-36
Diode Matrix	
Programmable Digital	227-68
Discriminator	
Direction	154-78
Window	1039-17
Disk	
Hard Disk Circuits	470-124
Pulse Detector	739-9
Winchester Disk Circuits	476-51
Display Controller–LCD	709-4
Display Drivers	
Bargraph	708-10
Electroluminescent	708-38
Gas Discharge	708-96
General	708-1
Lamp	708-107
LCD	708-109
LED	711-37
Plasma	712-34
TV Channel	851-86
Vacuum Fluorescent	712-59
Display Processor	465-113
Displays	942-66
Dividers	
Digital	
Special	226-54
Extender	227-1
PLL Circuits	814-61
DMA–Controllers	469-33
Dolby	832-83
DRAM's	
Controller	469-43
General Purpose	1247-1
Modules	1312-34
Video/Multiport	1358-46
Drivers	
Bridge	742-98
	744-17
Bus–See Line Drivers	
CMOS	130-84
Disk	738-25
Display	708-1
ECL	
10K	167-59
100K	172-66
FET	744-6
Fluorescent	712-59
Hammer	743-77
High Voltage	744-56
HNIL/HTL	177-5
Lamp	743-77
Latched	743-135
	744-114
LCD	708-109
LED	711-37
Line	717-1
Memory	738-1
MOSFET	742-125
	745-25
MOS Clock	733-21
MOS Memory	738-98
Motor	746-116
Peripheral	742-1
Plasma	712-34
Power	749-54

Function — Page-Line

Relay ... 750-21
Servo ... 750-33
Solenoid ... 743-31
... 750-61
Stepper Motors ... 743-32
... 749-29
... 750-67
TTL ... 202-131
DTMF–Telecom ... 1023-118
DUART
Data Bus Circuits ... 735-27
DVM Display ... 664-1
Dynamic RAM Controller ... 469-43
Dynamic RAM Memories ... 1247-1

E

EDTV ... 852-107
EEPROMs
Electrically Erasable ... 1209-1
Modules ... 1238-23
EISA ... 480-31
Electronic Volume Controls ... 837-20
Encoders
Television Circuits ... 852-115
Keyboard ... 716-1
Manchester ... 472-42
... 481-59
Encryption–See Data Encryption
EPROMs
UV Erasable ... 1137-1
Modules ... 1163-3
One-Time Programmable ... 1165-6
Error Checking Circuits ... 715-1
Error Correction ... 715-7
... 1019-10
Ethernet
General ... 469-63
... 1019-13

F

FAX Circuits ... 1032-51
FDDI ... 470-31
... 2204-28
FET Drivers ... 744-6

Function — Page-Line

Fiber Optics
Amplifier ... 939-82
FIFOs
CMOS ... 146-63
Memory ... 1103-1
TTL ... 215-45
Filters
Bandpass ... 1013-105
Baseband ... 1013-113
Butterworth ... 1014-113
Codec ... 1015-134
Comb ... 851-137
Digital ... 284-125
... 1013-102
FIR ... 227-15
... 285-22
Notch ... 1014-30
PCM ... 1016-106
SAW ... 1033-23
Switched Capacitor Array ... 1015-20
Fixed Point Processor ... 272-1
Flash Converter ... 612-5
Flash Memories
General Purpose ... 1173-1
Modules ... 1199-41
Flip Flops–See Digital Flip Flops
Floating Point Processor ... 278-1
... 480-70
Floppy Disk
Circuits ... 470-64
Controllers–See Controllers
Fluorescent Display Driver ... 712-59
FM–See Consumer Circuits
Followers ... 863-1
Frequency Counter ... 841-63
Frequency Synthesizer ... 814-79
Frequency to Voltage Converters ... 976-12
FSK
Modems ... 1030-21
PLL Circuits ... 815-60
Full-Bridge Power Driver ... 742-98
... 744-17
Function Generators ... 816-26
Fuse Programmable- PROMs
General Purpose ... 1129-1
Modules ... 1136-5

Gas Discharge - I/O

Function	Page-Line

G

Gas Discharge Display 708-96
Gates–See Digital
Gate Arrays 2036-1
Generator
- Baud Rate 226-1
- Bit Rate 154-52
- Color Bar 851-122
- Function 816-126
- Polynomial 715-35
- Sound 836-47
- Television Test Pattern 855-27
- Waveform 816-140

GPIB
- General 470-114
- TTL 221-110

Graphic Display Processor 470-120
Graphic Equalizer 832-111
Graphics Circuits 480-74
..... 2204-33
Ground Fault Interrupter 862-64

H

Hall Effect Devices
- Interface 744-38
- Linear 1011-12

Hard Disk Circuits 470-124
Histogram/Accumulating Buffer 480-105

I

IBM 360 Interface
- LIne Receivers 724-57

IBM 370 Interface
- Line Drivers 720-31
- Line Receivers 725-3

IEEE 802.3 1019-92
IF Amplifiers 841-71
..... 842-112
IGBT 744-64

Ignition–Automotive 838-89
Image Sensors 939-91
Industrial Time–Base Generator 154-96
Infrared Circuits 845-136
Injector Driver–Automotive 838-95
Instrumentation Amplifiers 864-1
Interface
- Analog Switches
  - Switches with Drivers 602-1
  - Switches without Drivers 606-45
  - Multiplexers 607-65
- Analog to Digital Converters
  - Binary 612-1
  - Decimal 664-1
- Digital to Analog Converters 665-1
- Display Drivers 708-1
- Error Checking Circuits 715-1
- Keyboard Encoders/Decoders 716-1
- Line Circuits
  - Data Bus Circuits 735-1
  - Drivers
    - RS-232 717-1
    - RS-422 717-29
    - RS-423 718-43
    - RS-485 719-1
    - General Purpose 719-29
    - Miscellaneous 720-30
  - Drivers/Receivers
    - RS-232 725-14
    - RS-422 729-14
    - RS-423 731-4
    - RS-485 731-22
    - General Purpose 733-14
    - Miscellaneous 733-42
  - Receivers
    - RS-232 720-42
    - RS-422 721-14
    - RS-423 722-36
    - RS-485 723-35
    - General Purpose 723-53
    - Miscellaneous 724-57
- Memory Drivers 738-1
- Peripheral Drivers 742-1
- Sense Amplifiers 752-1

Intermediate Frequency Amplifiers 726-25
I/O
- Controllers 480-113
- Expanders 480-115
- Ports 480-121

Function	Page-Line
Inverters–See Digital Inverters	
ISDN Circuits	1026-88
J	
JPEG Circuits	285-57
J-K Flip Flop–See Digital	
K	
Keyboard	
Controllers	471-77
Decoders	716-1
Encoders	471-108
	716-1
L	
Lamp Monitor	
Automotive	838-97
LAN	
Circuits	472-10
	481-37
	2205-31
Ethernet	464-101
Latches	
CMOS	142-92
ECL 10K	168-131
ECL 100K	173-64
TTL	213-103
LCD	
Controllers	472-5
	709-4
Drivers–See Display Drivers	
LED Drivers–See Display Drivers	
Level Shifters–See Translators	
Line Circuits	
Digital Bus Circuits	
BiCMOS	158-34
CMOS	110-79
ECL	164-39
TTL	182-114
General	717-1
Line Drivers	
RS-232	717-1
RS-422	717-29
RS-423	718-43
RS-485	719-1
General Purpose	719-29
Miscellaneous	720-30
Line Drivers/Receivers	
RS-232	725-14
RS-422	729-14
RS-423	731-4
RS-485	731-22
General Purpose	733-14
Miscellaneous	733-42
Line Receivers	
RS-232	720-42
RS-422	721-14
RS-423	722-36
RS-485	723-35
General Purpose	723-53
Miscellaneous	724-57
Linear	
Amplifiers	
Special Purpose	802-1
Arrays	
Transistor	808-1
Clock Circuits	811-1
Comparators	819-1
Consumer Circuits	830-1
Followers	863-1
Instrumentation Amplifiers	864-1
Operational Amplifiers	868-1
Optoelectronic Devices	939-1
Other Linear Devices	1035-1
Power Supply Circuits	949-1
Phase Locked Loops	814-61
Prescalers	817-13
Sensor Circuits	1011-1
Telecommunication Circuits	1013-1
Timers	1034-1
Link Adapter	466-42
Log Amplifiers	804-100
Log/Antilog Amplifiers	804-101
Logic–See Digital	
Logic Unit	
Digital	
CMOS	103-40
TTL	178-151
Look Ahead Carry–See Digital Arithmetic	
LVDT Converters	1036-83

Manchester - Microprocessor

Function	Page-Line
M	
Manchester Decoder/Encoder	
Interface	735-54
Microprocessors	472-42
	481-59
Mask ROMs	1115-1
Melody Circuit–Clock	840-30
Memory	
CAM	
ECL 10K	169-19
ECL 100K	173-74
Character Generators	1102-1
Controllers	482-1
Drivers	738-1
EEPROMs	
General Purpose	1209-1
Modules	1238-23
EPROMs	
UV Erasable	
General Purpose	1137-1
Modules	1163-3
One-Time Programmable	
General Purpose	1165-6
FIFOs	
CMOS	146-63
General	1103-1
TTL	215-45
Flash	
General Purpose	1173-1
Modules	1199-41
Multiport Register	147-37
Plug-In-Cards	1546-1
PROMs	
Fuse Programmable	
General Purpose	1129-1
Modules	1136-5
RAMs	
Dynamic	
General Purpose	1247-1
Modules	1312-34
Video/Multiport	1358-46
Static	
Cache Tag	1540-27
General Purpose	1365-1
Modules	1469-17
Multiport	1518-42
NOVRAMs	1532-39
Pseudostatic	1539-1
ROMs	
Mask Programmable	
General Purpose	1115-1
Speech	846-100
Simultaneous Read/Write	
Digital	215-66
TV	850-137
Memory Drivers	738-1
Meter–Level	1036-56
Microcontroller–See Microprocessor	
Microprocessor Development Systems	502-1
Microprocessors	
4-Bit	
1 MHz	302-1
2 MHz	302-2
4 MHz	302-8
8-Bit	
1 MHz	302-17
2 MHz	302-28
4 MHz	304-9
8 MHz	306-1
12 MHz	306-23
8/16-Bit	
4 MHz	308-4
8 MHz	308-7
12 MHz	308-23
16-Bit	
4 MHz	308-31
8 MHz	310-2
12 MHz	312-22
16 MHz	314-8
20 MHz	314-30
16/32-Bit	
8 MHz	316-17
12 MHz	316-23
16 MHz	316-25
20 MHz	316-35
32-Bit	
8 MHz	318-8
12 MHz	318-10
20 MHz	318-34
25 MHz	320-28
33 MHz	322-12
40 MHz	324-2
66 MHz	324-22

Function	Page-Line
90 MHz	324-30
32/64-Bit	
12 MHz	324-34
20 MHz	326-1
25 MHz	326-2
33 MHz	326-7
64-Bit	
50 MHz	326-12
90 MHz	328-1
Microcontrollers	
4-Bit	
0.1 MHz	330-1
1 MHz	332-17
2 MHz	334-3
4 MHz	334-43
6 MHz	342-36
8-Bit	
1 MHz	348-20
2 MHz	350-15
4 MHz	356-25
8 MHz	368-17
12 MHz	392-41
8/16-Bit	
4 MHz	436-36
8 MHz	436-37
16-Bit	
8 MHz	438-5
12 MHz	440-30
16 MHz	442-24
20 MHz	446-10
16/32-Bit	
8 MHz	452-22
12 MHz	452-26
16 MHz	452-33
20 MHz	452-37
32-Bit	
12 MHz	454-4
20 MHz	454-9
25 MHz	454-12
33 MHz	454-15
Microprocessor–System Components	
Bit Slice	
Macrologic Bipolar	456-1
Macrologic CMOS	456-3
4-Bit Slice	
2900	456-4
16-Bit Slice	
2900	456-53
1-Bit	
14500	456-55

Function	Page-Line
4-Bit	
1400	456-59
1500	456-74
2100	456-81
COP400	456-82
OLMS40	456-101
SM Series	456-112
TLCS470	456-117
TLCS47	457-20
TMS2000	457-60
*u*COM-75	457-62
Miscellaneous	457-66
8-Bit	
1650	457-70
1800	457-75
2650	458-47
3870	458-56
6000	458-81
6300	458-87
6500	458-124
6800	459-20
7000	460-43
8051	460-151
8080	461-47
8085A	462-11
8086/88	462-139
8088	462-146
8X300	462-148
Z8	463-3
Z80	463-64
Miscellaneous	464-46
8/16-Bit	
8086	464-49
8086/88	464-63
8088	464-147
9900	465-1
16000	465-14
80286	465-30
*u*COM-70K	465-31
12-Bit	
2900	465-38
2900 Controller	465-40
6100	465-46
16-Bit	
2900	465-49
6500	465-50
Z8000	465-51
8086	465-73
8096	465-75
16000	465-77

Mixer - Over/Under

Function	Page-Line
68000	465-87
TLCS68000	466-31
TMS380	466-36
Transputer	466-42
Z8000	466-56
16/32-Bit	
32000	466-60
80286	466-61
32-Bit	
32	466-89
32000	466-91
68000	467-4
80386	467-12
Transputer	467-42
Peripheral Controllers	467-63
General Purpose	477-18
Mixer	
Balanced	1032-99
Radios	841-106
PLL Circuits	815-62
Modem Circuits	1029-72
Modulator	
Pulse-Width	1003-6
Monitor	
Automotive Lamp	838-97
MOS Memory Drivers	738-98
MOSFET Drivers	742-125
	745-25
Motor Circuits	
Peripheral Drivers	746-60
Motor Speed Control	
Audio Tape Recorders	848-57
Motor Driver	748-10
Mouse Controller	472-89
MPU Development Systems	502-1
Multifunction Devices	2202-1
Multiplexer/Demultiplexer	227-37
Multiplexers	
Analog Switches	607-65
See Digital Multiplexers	
Multipliers–See Digital Multipliers	
Multivibrators	
CMOS	150-106
ECL III	175-21
ECL 10K	169-99
HNIL/HTL	177-15
TTL	218-78
Music	
Melody Generator	840-36
Sound Effect	840-130
Muting Circuits	833-52

N

NAND Gates–See Digital	
Network LAN–See LAN	
Neuron Chip	473-7
Nines Complementor-Digital CMOS	104-162
NOR Gates–See Digital	
NRZI–Encoder/Decoder	482-21
NTSC–TV	853-69
NOVRAMs	1532-39

O

Octal Buffers	106-178
One Time Programmable Memory–See PLD	
Operational Amplifiers	
Buffers	802-60
Characteristics	
Single	874-1
Dual	908-42
Triple	926-19
Quad	926-41
Chopper Stabilized	874-5
High Output Current	868-1
High Speed	868-75
High Voltage	869-17
Low Bias Current	870-1
Low Drift	871-26
Low Power	872-25
Wide Band	873-31
Optocouplers	942-119
Optoelectronic Devices	939-1
Optoisolators	944-15
OR Gates–See Digital	
Oscillators	
Crystal	1035-111
Numerically Controlled	227-42
Quadrature	1037-74
Over/Under Circuits	1007-73

Function	Page-Line

P

Pager Circuits..... 1032-117
..... 1037-77
PAL–TV..... 853-116
Palette..... 479-54
..... 857-23
Parity Generator–See Digital Arithmetic
PCM
Filter..... 1016-106
Repeater..... 1033-1
PCMCIA..... 473-55
..... 482-33
Peripheral Drivers..... 742-1
Phase Comparators..... 125-149
..... 815-63
Phase Control–AC..... 1035-4
Phase Locked Loop Circuits
Digital
CMOS..... 154-128
TTL..... 222-16
Linear..... 814-61
Photodetector–See Image Sensors
PIA..... 482-52
Pin Drivers..... 749-36
Pipeline Registers..... 284-27
Plasma Display Driver..... 712-34
PLD–See Programmable Logic Devices
PLL–See Phase Locked Loop
Plug-In-Cards
Memory..... 1546-1
Potentiometers..... 833-75
..... 1037-86
Power Amplifier Circuits..... 833-97
Power Factor Controller..... 1007-87
Power Supply–See Voltage Regulator
Power Supply Controller–See Voltage Sensors
Power Drivers
Full-Bridge..... 742-98
..... 744-24
Half-Bridge..... 742-99
..... 744-27
Preamplifiers
Audio Cassette Recorder..... 848-62
Remote Control..... 846-29
See Amplifiers
Special Purpose..... 805-33
Prefixes–See Part Number Guide
Prescalers
Count Extender..... 814-66
General..... 817-13
FM..... 845-6
Pressure Sensors..... 1011-129
Printer Circuits..... 749-136
Priority Encoder–See Digital Miscellaneous
Priority Interrupt Controller..... 482-69
Processor
Arithmetic
DSP..... 478-31
..... 480-6
Bilingual TV..... 851-12
Color TV..... 851-131
DSP..... 272-1
Fixed Point..... 480-2
Floating Point..... 480-70
TV..... 854-14
Programmable Diode Matrix..... 227-68
Programmable Logic Devices
Combinatorial Outputs
One-Time Programmable
..... 2102-1
..... 2109-1
Erasable Programmable
..... 2102-33
..... 2110-1
Registered Outputs
One-Time Programmable
..... 2103-1
..... 2112-1
..... 2140-1
Erasable Programmable
..... 2104-1
..... 2112-2
Electrically Erasable Prog.
..... 2112-15
Registered/Combinatorial Outputs
One-Time Programmable
..... 2109-1
..... 2140-1
Erasable Programmable
..... 2115-1
Electrically Erasable Prog.
..... 2124-3

Programmable Filter - RS485

Function — Page-Line

Superset
One-Time Programmable
.....2108-1
.....2131-41
.....2138-1
Erasable Programmable
.....2132-13
Electrically Erasable Prog.
.....2133-43
Static RAM.....2138-1
Programmable Filter
Interval/Timer.....466-82
Parallel Interface.....482-23
Tone/Noise Generator.....1024-88
PROMs
Fuse Programmable
General Purpose.....1129-1
Modules.....1136-5
Pulse Dialers.....1022-20
Pulse-Width Modulators.....1003-6

Q

Quad-Pole Analog Switches.....602-93

R

Radio Circuits
AM.....841-3
AM/FM.....841-35
FM.....842-63
Remote Control.....845-57
SSB.....841-24
Radio Frequency Amplifiers.....805-64
RAMs
Dynamic
General Purpose.....1247-1
Modules.....1312-34
Video/Multiport.....1358-46
Static
Cache Tag.....1540-27
General Purpose.....1365-1
Modules.....1469-17
Multiport.....1518-42
NOVRAMs.....1532-39
Pseudostatic.....1539-1

Function — Page-Line

RAMDACs.....474-16
.....482-115
Rate Multiplier
Digital–CMOS.....155-58
Read/Write Preamplifier.....740-46
Receivers
IR.....845-136
Line–See Line Circuits
Remote Control.....845-159
Recorder
Audio.....848-15
VCR.....849-24
Reed-Solomon Circuits.....285-81
.....468-32
.....715-7
Reference Voltage.....997-75
Registers
See Memory
See Digital Shift Registers
Regulators
Motor Speed.....749-11
Switching.....972-38
Relay Drivers.....750-12
Remote Control Circuits.....845-57
Resolver Systems.....1037-125
Ring Detector.....1033-21
RISC.....454-4
RF Circuits–See Linear Consumer
RGB Circuits.....854-23
.....859-60
ROMs–Mask Programmable.....1115-1
Row Drivers.....712-40
RS232
Line Drivers.....717-1
Line Drivers/Receivers.....725-14
Line Receivers.....720-42
RS422
Line Drivers.....717-29
Line Drivers/Receivers.....729-14
Line Receivers.....721-14
RS423
Line Drivers.....718-43
Line Drivers/Receivers.....731-4
Line Receivers.....722-36
RS485
Line Drivers.....719-1
Line Drivers/Receivers.....731-22
Line Receivers.....723-35

Function	Page-Line
S	
SAW Filter	1033-23
Sample and Hold Circuits	706-98
	1038-15
SBus Circuits	474-46
Schmitt Trigger–See Digital Inverters	
SCR Control	1038-17
SCSI	474-47
	483-26
SDLC–Microprocessor–9900	465-1
Security	1038-21
Sense Amplifiers	752-1
Serial Communication	475-7
Servo Circuits	1038-26
Shift Registers–See Digital Shift Registers	
Signal Processor	
DSP	272-1
Interface	483-48
Smoke Detector	862-87
	1038-48
SONET/SDH Circuits	1020-68
Sound Generator	836-47
SPARC Stations	2211-31
Speech Circuits	
Consumer	846-98
Processors	847-44
Telephone	846-141
Speed Control–Automotive	839-15
SRAMs	
Cache Tag	1540-27
General Purpose	1365-1
Modules	1469-17
Multiport	1518-42
NOVRAM	1532-39
Pseudostatic	1538-1
SSB Detector–Radio	841-24
Standard Cells	2072-1
Stereo	
AM	841-25
FM	845-30
TV	854-117
Strobe Light–Camera	839-96
Subscriber Circuits–See Telecommunications	
Successive Approximation	
Register	
CMOS	155-84
Microprocessor	483-73
Switches	
Analog	
with Drivers	602-1
without Drivers	606-45
Crosspoint	
Telecom	1017-80
Darlington	743-63
	751-43
Hall Effect	744-38
	1011-38
Multiplexers	607-65
Touch	
Linear	1038-108
Video	861-87
Switching Regulator Circuits	1008-146
Synchro Systems	1038-68
Synthesizers	
AM/FM	841-127
Frequency	814-79
General	1032-74
Music	840-61
Speech	847-59
TV	855-38
T	
T1 Circuits	1029-40
Tachometer Circuit	839-22
Tape Recorder Circuits	
Audio	848-15
Video	849-24
Telecommunication Circuits	
Active Filters	1013-1
Bell 103/212/208A/B	1029-90
Codecs	1015-119
Compandors	1017-34
Crosspoint Switches	1017-70
Data Communications	1018-3
Dialers	1021-100
DTMF Generators/Receivers	1023-118
Line Interface Circuits	1025-23
Modem Circuits	1029-72
Modulators	1031-68
Miscellaneous	1031-76

Telephone - VGA

Function	Page-Line
Subscriber Circuits	1027-101
Telephone	
Answering Device	1032-33
Cordless	1031-98
Digital Circuit	1032-36
FAX	1032-51
Teletext Circuits	855-22
Television Circuits	
NTSC/PAL Circuits	853-70
PAL/NTSC Circuits	853-118
Remote Control	854-20
RGB Circuits	854-23
Sound	854-78
Sync	854-124
Tuner	855-30
Vertical	855-83
Video Circuits	855-120
Temperature–Transducers	1012-84
Test Pattern Generator–TV	855-27
Thermocouple	1038-88
Timers	
Counter/Timer	226-17
Digital	155-93
Linear-555	1034-31
Token Ring Circuits	466-36
Tone Decoders	
PLL Circuits	816-107
Telecom	1024-59
Tone/Pulse Dialers	1023-31
Tone Generator	
Music	841-1
Telecom	1024-88
Touch Switches–See Switches	
Track and Hold Amplifiers	1038-112
Traffic Camera–TV	855-29
Traffic Information - Automotive	838-18
Transceivers	
Bus	
CMOS	110-79
TTL	182-136
Line	725-14
Transducers	
Pressure	1011-129
Temperature	1012-84
Transistor	
Arrays	808-1
Matched	808-6
Translators	
CMOS	154-7
ECL 10K	169-122
TTL	221-3
Transmitters	
IR	846-22
Remote Control	846-18
Transputer	466-42
	467-42
TRIAC Control	1038-17
Trigger	
See Schmitt Trigger	
Zero Crossing	1039-18
Tuner	
AM	841-32
AM/FM	842-44
FM	845-50
TV	855-30

U

UART	
Microprocessor	
General	484-28
Transmitters-Receivers	735-26
***u*-Law**	
Linear	1015-128
UV Erasable Memory	
Modules	1163-3
One-Time Programmable	1165-6

V

V.21	1029-105
V.22	1030-63
V.26	1030-74
V.29	1030-76
V.32	1030-78
V.33	1030-84
VCO	
ECL III	175-33
Generators	
Function	816-126
Waveform	816-140
PLL Circuits	815-71
TTL	224-16
VGA Circuits	484-57

Function	Page-Line
Video	
Amplifier	856-116
	860-20
Controller	476-10
CRT	479-83
DAC	476-15
	484-68
Decoder	857-130
	2211-1
Delay Line	852-68
Display Driver	860-98
Encoder	858-23
	860-109
Multiplexer	859-1
	861-19
Processor	476-19
	859-51
	861-55
Switches	861-87
Video Circuits–TV	855-120
Viterbi	1021-65
VMEbus Circuits	484-76
Vocabulary–Speech Circuit	847-59
Voice	
Processor	847-44
Recognition Circuit	847-136
Scrambler	846-142
Synthesizer	848-1
Voltage Alarm	995-1
Voltage Controlled Amplifier (VCA)	837-20
Voltage Controlled Oscillator (VCO)	
	See VCO
Voltage Converters	
AC-DC	976-12
DC-DC	977-1
Voltage Detectors	995-1
Voltage Doublers	1009-49
Voltage Inverters	1009-49
Voltage Monitors	995-1
Voltage Regulators	
Adjustable	
Dual	972-27
Negative	971-101
Positive	968-49
Automotive	839-37
Fixed	
Dual	968-2
Negative	965-34
Positive	949-1
Switching Regulator Circuits	972-38
Voltage References	997-75
Voltage Sensors	1001-115
Volume Control	837-30

W

Watch–Consumer	839-104
Watchdog Timers	484-92
Waveform Generators	816-140
WidebandAmplifiers	806-92
	873-32
Winchester Circuits	476-50
	740-133
Workstations	2211-31

X

X.25 Protocol Controller	477-8
XGA Chip Set	2205-20

Z

Zero Crossing Triggers	1039-18

INTRODUCTION TO DIGITAL

Digital devices are listed by major product families: BiCMOS, CMOS, ECL, GaAs, or TTL, and within them by functional groups such as arithmetic, buffers and inverters.

A few digital devices, such as watch, clock, speech and music circuits, are not covered in the digital section, but are included in the Linear – Consumer Circuits guide.

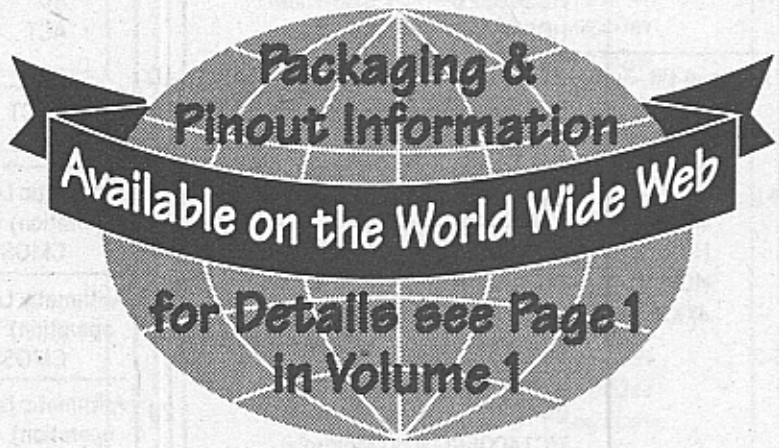

Digital Logic Topics

CMOS.....102
BiCMOS 157
ECL 10K.....164
ECL 100K.....171
ECL 101K.....174
GaAs 176
HNIL/HTL.....177
TTL 178
Special.....226

ICS Chips . . . They're Everywhere!

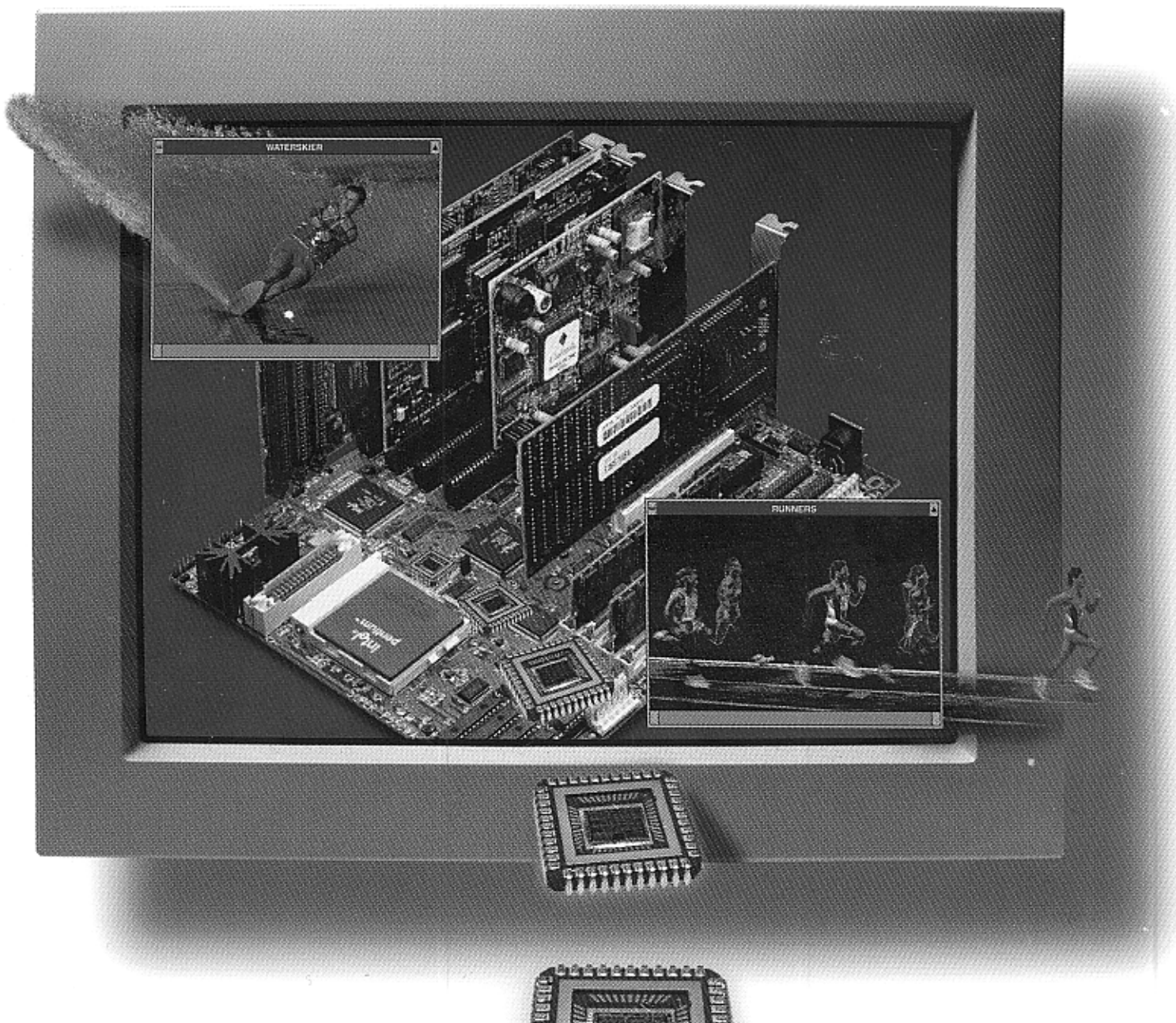

Leader in Mixed-Signal Chips

For 20 years (1976-1996), Integrated Circuit Systems (ICS) has been a leader in high-performance, CMOS, mixed-signal ICs.

Clock Chips

ICS, the undisputed leader in clocks, has the right clock for motherboards built with any μP's and chip sets. Microprocessors include: 486, Pentium,™ Nx586,™ Power PC™ and P6. And chip sets from Intel, Opti, PicoPower, SIS and VLSI. Also, clocks for: Rambus,™ digital video, digital set-tops, modems, disk drives and printers.

Network Chips

ICS's high-performance PHYceiver™ chips are used internationally in the latest network systems. The chips work in LAN and WAN systems, especially the newest technologies like: SONET/SDH fiber optic systems, ATM copper/fiber systems and Fast Ethernet systems.

Multimedia Chips

ARK Logic's* devices provide OEMs with world-class chips for 32/64-bit graphic cards; full-motion video playback and multiple windows; 3D animation in real time; and graphics, video and 3D on one chip for CAD, graphic arts, spreadsheets and game applications.

ASIC Chips

ICS's mixed-signal chips integrate sophisticated analog functions and high integration digital logic. Design strengths include: data acquisition, frequency synthesis, switched capacitors, PLL/VCO, embedded microcontrollers and DSP. Designs are foundry mobile for greater manufacturing flexibility.

Information

Check out our web site or call for samples, demo boards, catalog, short form, CD-ROM, application engineers, rep/dist lists, etc.
Call 1-800-220-3366 or http://www.icsinc.com.

Integrated Circuit Systems
http://www.icsinc.com

ARK Logic, Inc.
1737 North First Street, Suite 680
San Jose, CA 95112
408-467-1988

ICS Silicon Valley Headquarters
1271 Parkmoor Avenue
San Jose, CA 95126-3448
408-297-1201

ICS Corporate Headquarters
2435 Boulevard of the Generals
P.O. Box 968
Valley Forge, PA 19482-0968
610-630-5300

*ICS owns a majority interest in ARK Logic.

All registered marks and trademarks are the property of their respective owners.

1997
VOLUME 2

SELECTION GUIDES AND ALTERNATE SOURCES

IC MASTER

MASTER SELECTION GUIDES II
- **ASIC/Custom**
- **Programmable Logic Devices**
- **Chip Sets and Multifunction**

- **Military Parts Directory**
- **Application Note Directory**
- **Alternate Source Directory**

VOLUME 1
Selection Guides I
Function Index

VOLUME 3
Manufacturers and Distributors Directory
Part Number Guide
Part Number Index
Advertisers Technical Data

Hearst Business Publishing/UTP Division

INTRODUCTION TO ASIC/CUSTOM CIRCUITS

This section describes ASIC/Custom products. The first guide lists custom capabilities; the subsequent guides cover devices.

Category

Capabilities Charts.....2010
Gate Arrays.....2036
Linear and Linear/Digital Arrays.....2068
Standard Cells.....2071

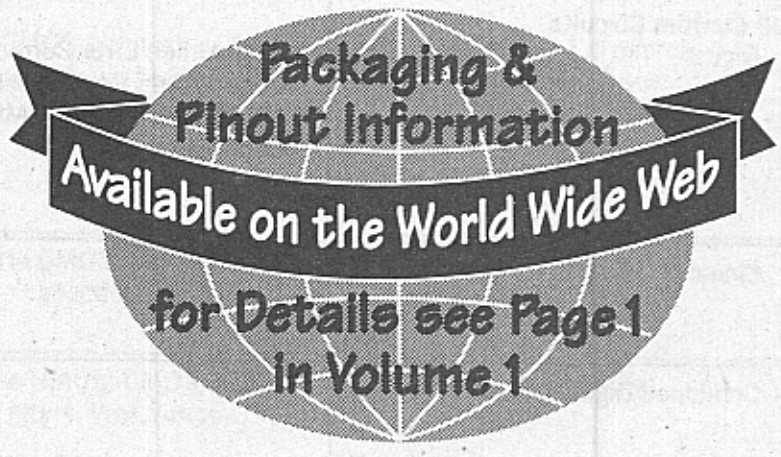

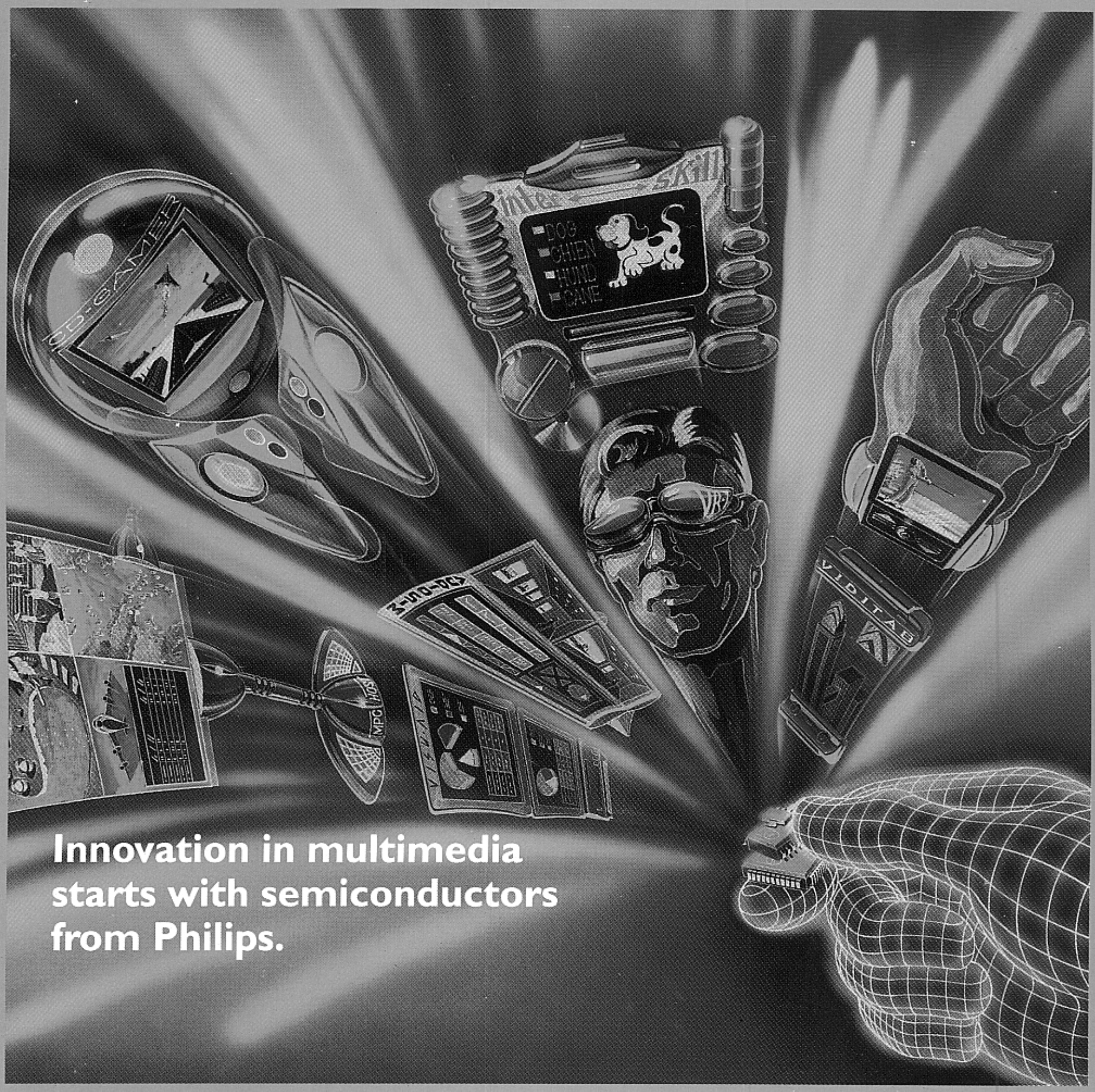

Let's make things better.

Philips Semiconductors

Nobody does more to help you unlock the potential of multimedia.

We've got the semiconductors to fire your imagination. There's a full-motion MPEG-1 video and audio decoder. An interface chip for low-cost video capture via the PCI-bus. Plus our next-generation TriMedia DSP, complete with programmable VLIW architecture, coming soon.

If you're ready to invent the future, we're ready to help. Ask for our latest Briefing on Multimedia Semiconductors.

Call: 1-800-447-1500, ext. 1163.

PHILIPS

PHILIPS

1997
VOLUME 3

MANUFACTURERS DIRECTORY AND TECHNICAL DATA

IC MASTER

- Manufacturers and Distributors Directory
- Part Number Guide
- Part Number Index
- Advertisers Technical Data

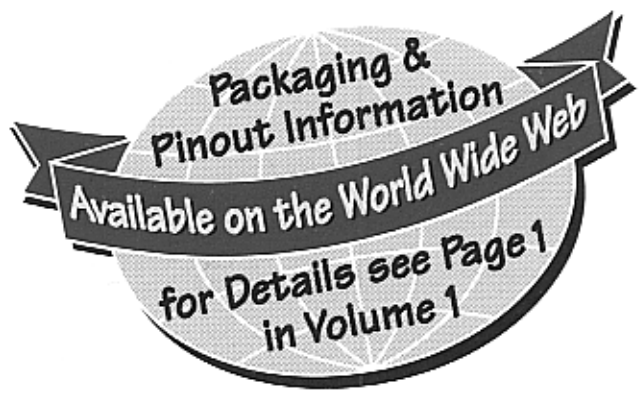

VOLUME 1
Selection Guides I
Function Index

VOLUME 2
Selection Guides II
Military Parts
Application Notes
Alternate Source Directory

Hearst Business Publishing/UTP Division

Volume 1

Mitsubishi .....(Inside Front Cover)
National Semiconductor ..... IFC Insert (R.H.)
Classic Components... IFC Insert (L.H.)
Nu Horizons .....(Opposite Table of Contents)
Registration 1
Contents 3
IC MASTER Staff 4
How to use the IC MASTER 4
Editorial Advisory Board 7
Abbreviations of Company Names 8
Master Selection Guide Function Index 11
Digital Selection Guide 101
Digital Signal Processors 271
Processor/Controllers Selection Guide 301
Microprocessor Development Systems 501
Interface Selection Guide 601
Linear Selection Guide 801
Memory Selection Guide 1101
Classic Components .....(Inside Back Cover)
Integrated Circuit Systems .....(Back Cover)
Technology Multi Sources .....(Inside Back Cover)

Volume 2

Classic Components .....(Inside Front Cover)
National Semiconductor ..... IFC Insert (R.H.)
Nu Horizons .....(Opposite Table of Contents)
Contents 2001
IC MASTER Staff 2002
Micronix Integrated Systems .....(Opposite ASIC)
Lansdale .....(Opposite ASD)
How to use the IC MASTER ... 2002
Editorial Advisory Board 2005
Abbrev. of Company Names ... 2006
ASICS/Custom Selection Guide...2009
Programmable Logic Devices Selection Guide 2101
Chip Sets and Multifunction Devices 2201
Military Parts Directory 2221
Application Note Directory 2352
Lansdale Semiconductor 2500
Alternate Source Directory 2501
Wing Shing .....(Inside Back Cover)
Philips Semiconductor .....(Back Cover)

Volume 3

KOH Electronics ...(Inside Front Cover)
National Semiconductor ..... IFC Insert (R.H.)
Classic Components .....IFC Insert
Contents 3001
IC MASTER Staff 3002
How to use the IC MASTER ... 3002
Editorial Advisory Board 3005
Abbrev. of Company Names ... 3006
Company Mergers, Acquisitions and Changes.....3008
Manufacturers and Distributors Directory 3009
Part Number Guide 3201
Part Number Logo Finder 3202
Part Number Index 3301
Advertisers Data Pages 3801
Actel 3801
Aeroflex Circuit Technology 3807
AKM 3808
Allegro Microsystems 3814
Alpha Semiconductor 3816
Analog Devices.....3821
Apex 3835
Applied Micro Circuits 3839
Astec Semiconductor 3840
Benchmarq 3841
Burr Brown 3845
Dallas Semiconductor.....3872
Data Delay Devices 3880
Datel 3883
Ericsson Components 3888
Excel Micro 3890
G-Link 3895
Harris Semiconductor.....3896
IC Works 3903
ICT 3910
Integrated Circuit Systems.....3905
Intel 3911
Lansdale Semiconductor 3927
LSI 3943
Micrel 3948
Micro Networks 3956
Micronix Integrated Systems 3960
Mitsubishi Electronics 3961
Mosel-Vitelic 3968
MSIS Semiconductor 3973
National Instruments 3974
National Semiconductor.....3975
Nexcom 3988
Nippon Precision Circuits 3990
NJR Corp. 3994
NPNX 3996
Pericom Semiconductor 3998
Philips Semiconductor 4003
RICOH Corp. 4056
Rochester Electronics 4061
Rohm Electronics.....4063
Samsung Semiconductor 4071
Seiko Instruments 4093
Semtech Corp. 4094
Seponix 4100
SGS Thomson 4101
Sharp Electronics.....4127
Siemens Components 4137
Synergy Semiconductor 4138
Syntaq Technology 4141
TDK Semiconductor 4142
Toshiba America 4147
USAR 4175
Western Design Center 4176
White Microelectronics 4177
Xilinx 4179
Yamaha 4189
Wing Shing .....(Inside Back Cover)
Classic Components .....(Back Cover)
NuHorizons.....(Inside Back Cover)

© Copyright 1997. Hearst Business Communications, Inc.
All Rights Reserved.

ISSN # 0894-6809